

MTech
MASTERCLASSES
in TECHNOLOGY
Imagine • Design • Build
www.mtech.mathscitech.org
07492 896846


Tiny Booster: 3V to 5V converter

Layout

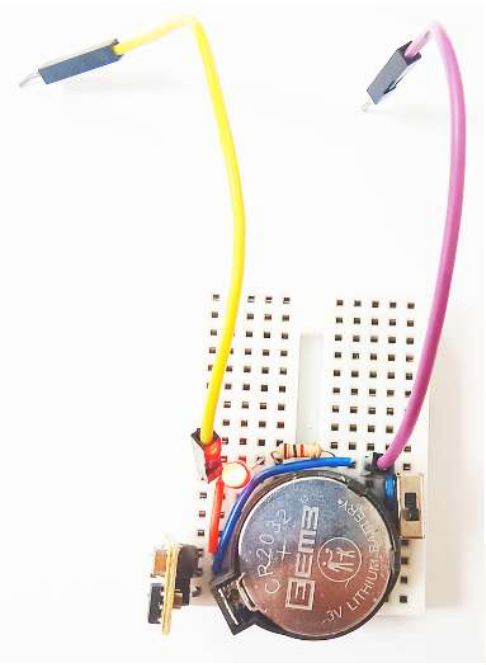

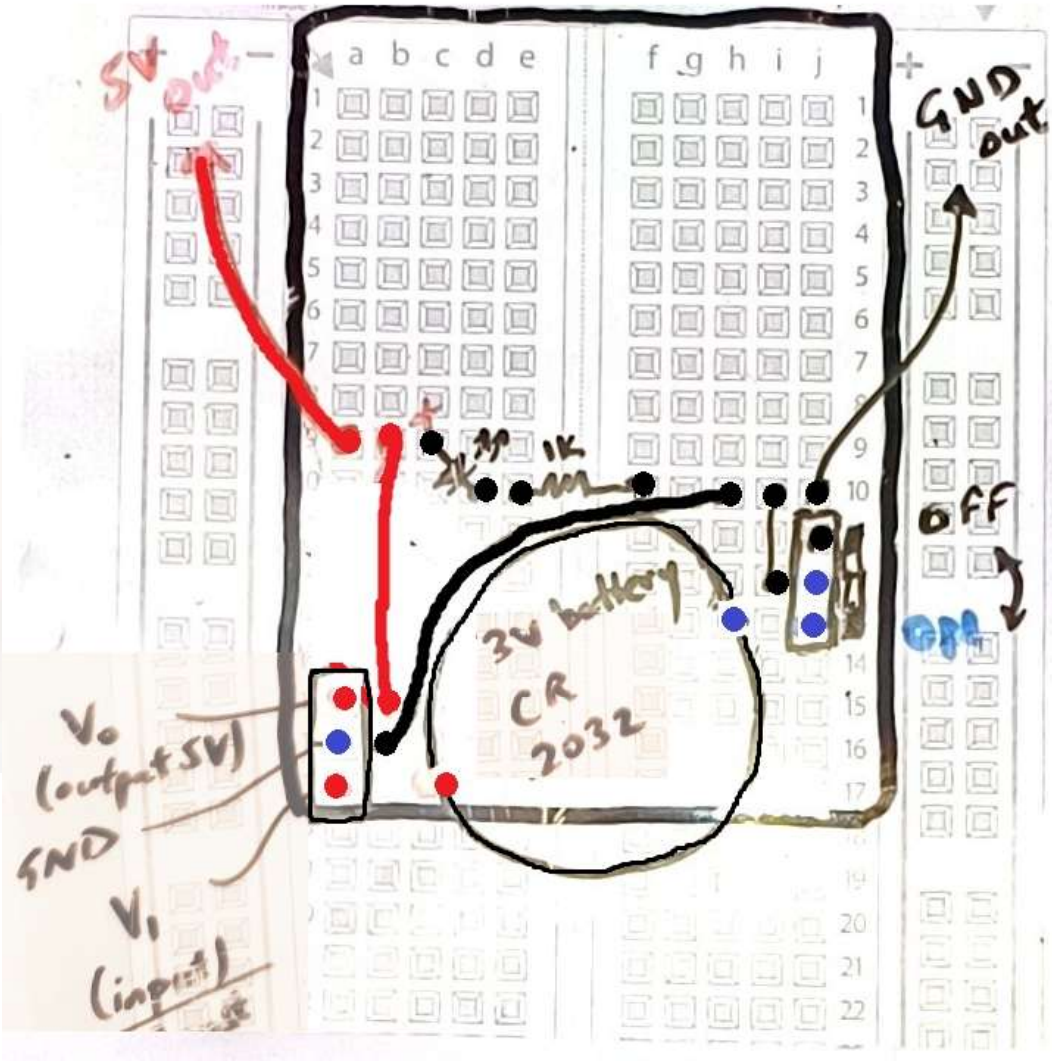

Schematic

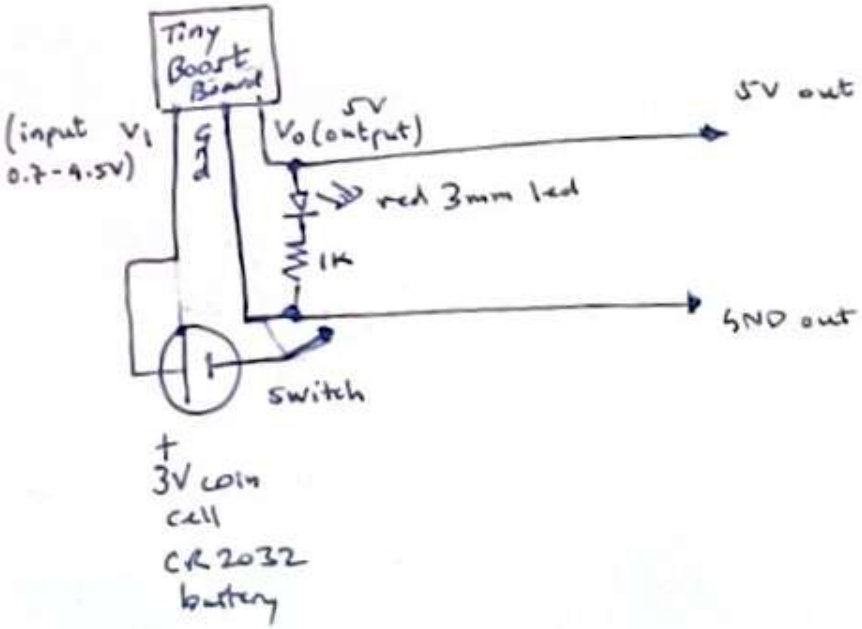

Specifications: *measure with multimeter*

Current Draw:
- When OFF:
  - 0 mA
- When ON:
  - 0.1 mA no LED (no 5V load)
  - 6.5 mA through the LED (no 5V load)

Voltage:
- 4.98 regulated voltage out